

Broj indeksa:

Ime i prezime:

Marina


Kombinacija broj:

1

1.

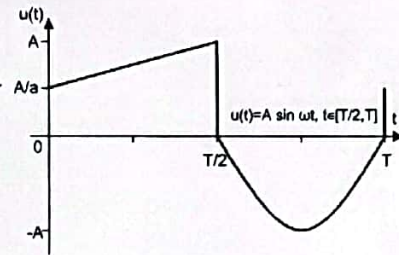**ZADATAK IZ ZBIRKE**

Napon talasnog oblika kao na slici, dovodi se na voltmetar sa kretnim kalemom i jednostranim ispravljačem, podešen da pokazuje efektivnu vrednost sinusnog napona. Odrediti apsolutnu vrednost relativne greške merenja efektivne vrednosti datog napona ovim voltmetrom.  $A = 4.5 \text{ V}$ ,  $a = 1.5$ ,  $f = 52 \text{ Hz}$ .



Odgovori:  a 19.31%  b 5.70%  c 8.87%  d 13.19%  e 3.31% (16 bodova)

2.

Otpornik nepoznate otpornosti  $R_x$  se meri U/I metodom, naponskim spojem. Kada se za merenje napona u ovoj metodi koristi voltmetar sa mekim gvoždem, klase tačnosti 1.0 i unutrašnje otpornosti  $2500 \Omega$ , ampermetar sa kretnim kalemom, opsega  $1.2 \text{ mA}$ , pokazuje  $0.5 \text{ mA}$ . Kada se umesto prvog, veže drugi voltmetar, klase tačnosti 0.5 i unutrašnje otpornosti  $1000 \Omega$ , ampermetar pokazuje  $0.6 \text{ mA}$ . Za ampermetar, unutrašnje otpornosti  $120 \Omega$ , smatramo da meri sa zanemarivom greškom. Kolo se napaja iz idealnog izvora jednosmernog napona. Odrediti vrednost  $R_x$ .

Odgovori:  a 7786  $\Omega$   b 2214  $\Omega$   c 544  $\Omega$   d 3968  $\Omega$   e 1205  $\Omega$  (16 bodova)

3.

Kolika je kombinovana merna nesigurnost paralelne veze dva otpornika čiji je odnos otpornosti 4, a standardne merne nesigurnosti otpornika su jednake i iznose 1 %?

Odgovori:  a 0.71%  b 0.82%  c 0.85%  d 0.75%  e 0.79% (16 bodova)

**ZADATAK IZ ZBIRKE**

4.

Za koliko se promeni struja mikroampermetra u naizmeničnom mostu u okolini ravnotežnog stanja, kada dođe do promene vrednosti induktivnosti  $L$  za 1.0 %?

$R_1 = 0.5 \text{ k}\Omega$ ,  $R_2 = R_3 = 1 \text{ k}\Omega$ ,  $R_4 = 2 \text{ k}\Omega$ ,  $L = 100 \text{ mH}$ ,  $C = 100 \text{ nF}$ ,  $U = 3 \text{ V}$ ,  $f = 50 \text{ Hz}$ .

Odgovori:  a 40 nA  b 4 nA  c 200 nA  d 20 nA  e 400 nA (16 bodova)






2.  $R_x = ?$  UI metoda naponski spoj

— (A) KK  $I_{max} = 1,2 \text{ mA}$   
 $R_A = 120 \Omega$   $I_1 = 0,5 \text{ mA}$

— (V1) MG  $kl_{V1} = 1\%$   
 $R_{V1} = 2500 \Omega$

— (V2)  $kl_{V2} = 0,5\%$   
 $R_{V2} = 1000 \Omega$

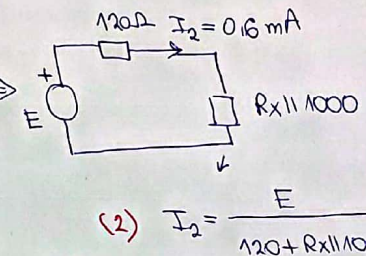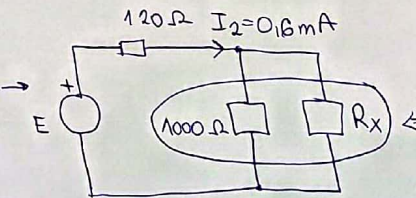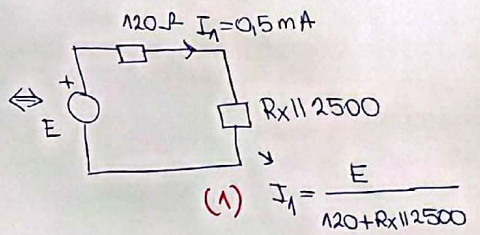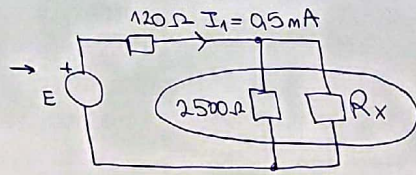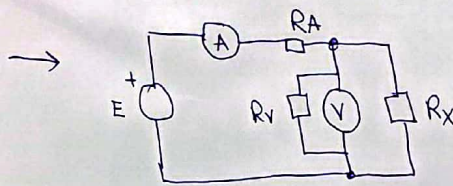— (A) KK  $I_{max} = 1,2 \text{ mA}$   
 $I_2 = 0,6 \text{ mA}$



(1) 
$$I_1 = \frac{E}{120 + R_x \parallel 2500}$$

(2) 
$$I_2 = \frac{E}{120 + R_x \parallel 1000}$$

$$\frac{10}{10} \cdot \frac{0,5 \text{ mA}}{0,6 \text{ mA}} = \frac{120 + R_x \parallel 1000}{120 + R_x \parallel 2500}$$

$$\frac{5}{6} = \frac{120 + R_x \parallel 1000}{120 + R_x \parallel 2500}$$

$$5 \cdot (120 + 2500 \parallel R_x) = 6 \cdot (120 + 1000 \parallel R_x)$$

$$600 + 5(2500 \parallel R_x) = 720 + 6(1000 \parallel R_x)$$

$$600 + 5 \cdot \frac{2500 \cdot R_x}{2500 + R_x} = 720 + 6 \cdot \frac{1000 \cdot R_x}{1000 + R_x}$$

$$\frac{12500 R_x}{2500 + R_x} = 120 + \frac{6000 R_x}{1000 + R_x} \quad /: 10$$

$$\frac{1250 R_x}{2500 + R_x} = 12 + \frac{600 R_x}{1000 + R_x}$$

$$\frac{1250 R_x}{2500 + R_x} = \frac{12(1000 + R_x) + 600 R_x}{1000 + R_x}$$

$$\frac{1250 R_x}{2500 + R_x} = \frac{612 R_x + 12000}{1000 + R_x}$$

$$1250 R_x \cdot (1000 + R_x) = (2500 + R_x)(612 R_x + 12000)$$

$$1250000 R_x + 1250 R_x^2 = 1530000 R_x + 30000000 + 612 R_x^2 + 12000 R_x$$

$$638 R_x^2 - 292000 R_x - 30000000 = 0$$

$$R_{x1,2} = \frac{292000 \pm \sqrt{8,5264 \cdot 10^{10} + 4,656 \cdot 10^{10}}}{1276}$$

$$R_{x1,2} = \frac{292000 \pm 4,02273538 \cdot 10^5}{1276}$$

$$R_{x1,2} = \frac{292000 \pm 402273,538}{1276}$$

$$\Rightarrow R_{x1} = 544,1015 \Omega$$

$$R_{x2} = -86,4212 \Omega \quad \downarrow$$


$$\Rightarrow R_{x1} = 544 \Omega$$

$$\boxed{3.} \quad \frac{u(R_{EKV})}{R_{EKV}} = ?$$

$$\frac{u(R_1)}{R_1} = 1\% \Rightarrow \frac{u(R_1)}{R_1} = 0,01 \Rightarrow u(R_1) = 0,01 \cdot R_1 \stackrel{*}{=} 0,01 \cdot 4R_2 = 0,04R_2$$

$$\frac{u(R_2)}{R_2} = 1\% \Rightarrow \frac{u(R_2)}{R_2} = 0,01 \Rightarrow u(R_2) = 0,01 \cdot R_2$$
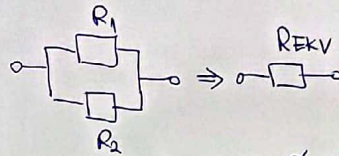
$$\frac{R_1}{R_2} = 4 \Rightarrow \boxed{R_1 = 4R_2}^*$$



$$R_{EKV} = \frac{R_1 R_2}{R_1 + R_2} \stackrel{*}{=} \frac{4R_2^2}{5R_2} = \frac{4}{5} R_2$$

$$\frac{\partial R_{EKV}}{\partial R_1} = \frac{R_2(R_1 + R_2) - R_1 R_2}{(R_1 + R_2)^2} = \frac{R_2^2}{(R_1 + R_2)^2}$$

$$= \left( \frac{R_2}{R_1 + R_2} \right)^2 \stackrel{*}{=} \left( \frac{R_2}{5R_2} \right)^2 = \frac{1}{25}$$

$$\frac{\partial R_{EKV}}{\partial R_2} = \frac{R_1(R_1 + R_2) - R_1 R_2}{(R_1 + R_2)^2} = \frac{R_1^2}{(R_1 + R_2)^2}$$

$$= \left( \frac{R_1}{R_1 + R_2} \right)^2 \stackrel{*}{=} \left( \frac{4R_2}{5R_2} \right)^2 = \frac{16}{25}$$

$$u(R_{EKV}) = \sqrt{\left( \frac{\partial R_{EKV}}{\partial R_1} \right)^2 u^2(R_1) + \left( \frac{\partial R_{EKV}}{\partial R_2} \right)^2 u^2(R_2)}$$

$$u(R_{EKV}) = \sqrt{\left( \frac{1}{25} \right)^2 (0,04R_2)^2 + \left( \frac{16}{25} \right)^2 (0,01R_2)^2} = \sqrt{\frac{1}{25^2} \cdot 0,0016R_2^2 + \frac{256}{25^2} \cdot 0,0001R_2^2}$$

$$u(R_{EKV}) = \sqrt{\frac{R_2^2}{25^2} (0,0016 + 0,0256)} = \frac{R_2}{25} \sqrt{0,0272} = \frac{\sqrt{0,0272}}{25} \cdot R_2$$

$$\frac{u(R_{EKV})}{R_{EKV}} = \frac{\frac{\sqrt{0,0272} \cdot R_2}{25}}{\frac{4}{5} \cdot R_2} = \frac{\sqrt{0,0272}}{20} = 0,008246$$

$$\Rightarrow \frac{u(R_{EKV})}{R_{EKV}} \cdot 100\% = 0,8246\%$$

$$\Rightarrow \frac{u(R_{EKV})}{R_{EKV}} \cdot 100\% = 0,82\%$$