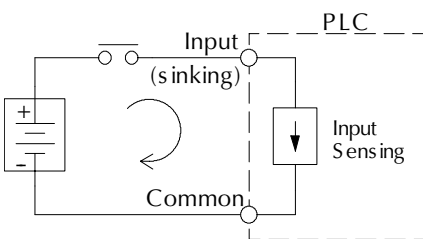


SINKING AND SOURCING CONCEPTS

When choosing the type of input or output module for your system (or DL05/DL06/DL105 I/O type), it is very important to have a solid understanding of sinking and sourcing concepts. Use of these terms occurs frequently in input or output circuit discussions. It is the goal of this section to make these concepts easy to understand, so you can make the right choice the first time when selecting the type of I/O points for your application. This section provides short definitions, followed by general example circuits.

First you will notice that the diagrams on this page are only associated with DC circuits and not AC, because of the reference to (+) and (-) polarities. *Therefore, sinking and sourcing terminology only applies to DC input and output circuits.* Input and output points that are sinking or sourcing can conduct current in one direction only. This means it is possible to connect the external supply and field device to the I/O point, with current trying to flow in the wrong direction, and the circuit will not operate. However, the supply and field device can be connected every time by understanding sourcing and sinking.


The figure below depicts a *sinking* input. To properly connect the external supply, it must be connected so the input provides a path to supply common(-). So, start at the PLC input terminal, follow through the input sensing circuit, exit at the common terminal, and connect the supply (-) to the common terminal. By adding the switch between the supply (+) and the input, the circuit is completed. Current flows in the direction of the arrow when the switch is closed.




Sinking = provides a path to supply **common (-)**

Sourcing = provides a path to supply **source (+)**


Sinking Input
(IEC: positive logic)

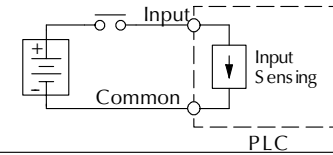


Sinking Output
(IEC: negative logic)

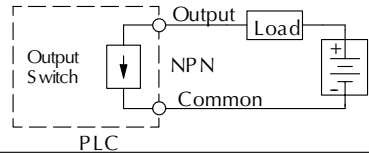

Sourcing Input
(IEC: negative logic)

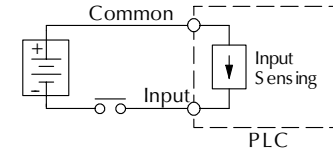

Sourcing Output
(IEC: positive logic)

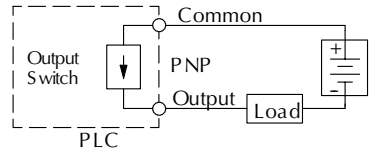


By applying the circuit principles to the four possible combinations of input/output sinking/sourcing types, there are four circuits, as shown above. The common terminal is the terminal that serves as the common return path for all I/O points in the bank.


Sink/source I/O circuits combine sinking and sourcing capabilities. This means that the I/O circuitry in the PLC will allow current to flow in either direction, as shown to the right. The common terminal connects to one polarity, and the I/O point connects to the other polarity (through the field device). This provides flexibility in making connections to your field power supply. Please note:

- Wire all I/O points with a shared common as either sinking or sourcing.
- Do not use an AC power supply on a DC sink/source I/O point.

Sink/Source Input
(IEC: pos./neg. logic)

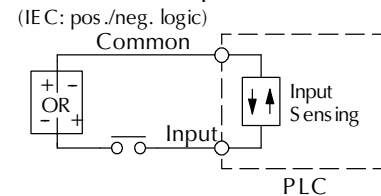


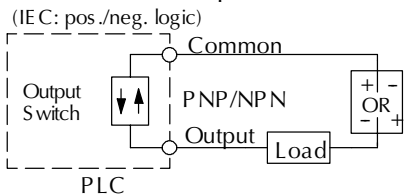Sink/Source Output
(IEC: pos./neg. logic)




Field device examples - 3 wire connections

NPN (Sinking)
Field Device Example

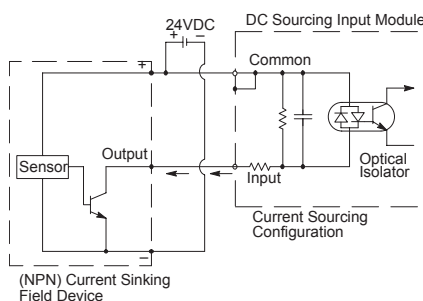

PNP (Sourcing)
Field Device Example

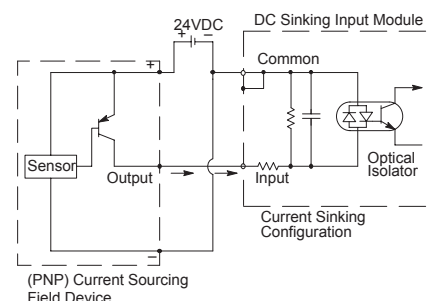



SINKING AND SOURCING CONCEPTS

Common terminals and how to use them

In order for a PLC I/O circuit to operate, current must enter at one terminal and exit at another. This means at least two terminals are associated with every I/O point. In the figure to the right, the input or output terminal is the main path for the current. One additional terminal must provide the return path to the power supply. Together, the main path and the return path create a loop, or a *complete circuit* for current to flow.

If there was unlimited space and budget for I/O terminals, then every I/O point could have two dedicated terminals. However, providing this level of flexibility is not practical or even necessary for most applications. So, most input or output points on PLCs are in groups that share the return path (called *commons*). The figure to the right shows a group (or bank) of four input points that share a common return path. In this way, the four inputs require only five terminals instead of eight.

NOTE: Assuming all input circuits have a similar resistance, the current at the common terminal is four times greater than the current at any one of the inputs. This effect is especially important to note for output circuits, where the current through a common terminal can reach several amperes. You will need to decide whether to fuse each output point individually, or to put a fuse in the common terminal path.

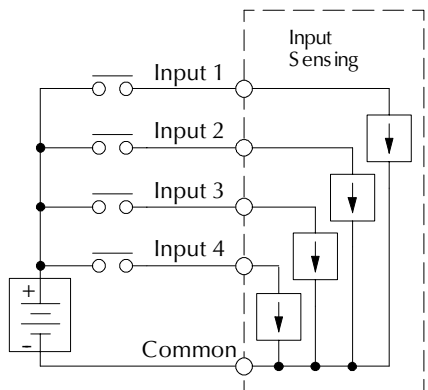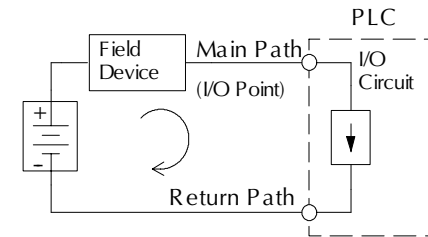


DL05/DL06/DL105 — Most DL05, DL06 and DL105 input and output circuits are grouped into banks that share a common return path. The best indication of I/O common grouping is on the wiring label. Sample DL05, DL06 and DL105 wiring labels and their meanings are shown below.

Wiring labels and how to interpret them

DL205, DL305, DL405 - Most DL205, DL305 and DL405 input and output modules group their I/O points into banks that share a common return path. The best indication of I/O common grouping is on the wiring label, such as the one shown to the right. The miniature schematic shows two circuit banks with eight input points in each. The common terminals are labeled “CA” and “CB,” respectively.


In the wiring label example, the positive terminal of a DC supply connects to the common terminals. Some of the symbols you will see on wiring labels and their meanings are shown to the right.

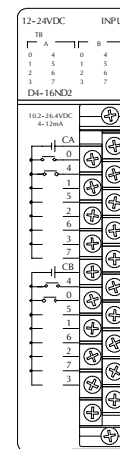- AC supply
- AC or DC supply
- DC supply
- Input Switch
- Output Load



DL405 input module shown


Input Bank (DL05)

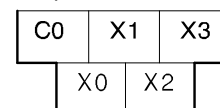

I/O Common Grouping Bar (DL105)



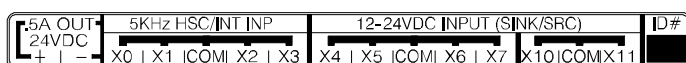Two banks of four inputs and one bank of two (DL105)



Two banks of four inputs and two banks of three outputs (DL05)

AC(I)	AC(N)	C0	X1	X3	X4	X6	C2	Y1	Y3	Y5	
	G ⊕	LG	X0	X2	C1	X5	X7	Y0	Y2	Y4	C3

SINKING AND SOURCING CONFIGURATIONS

The tables on the following pages summarize sinking and sourcing configurations for the DL05, DL06 and DL105 PLCs, and the DL205, DL305, and DL405 I/O modules. For more detailed information, see the corresponding data sheets in the related sections of this desk reference that cover each PLC and/or I/O module.

Sinking/Sourcing Configurations										
Modules	DC Current Sourcing IN	DC Current Sourcing OUT	DC Current Sinking IN	DC Current Sinking OUT	DC Current Sink/Source IN	AC/DC Current Sink/Source IN	AC/DC Sink/Source (Relay) OUT	AC IN	AC OUT	
DL05	D0-05AR						✓	✓		
	D0-05DR					✓	✓			
	D0-05AD			✓				✓		
	D0-05DD			✓		✓				
	D0-05AA							✓	✓	
	D0-05DA					✓			✓	
	D0-05DD-D				✓	✓				
	D0-05DR-D					✓		✓		
DL06	D0-06AA							✓	✓	
	D0-06AR						✓	✓		
	D0-06DA					✓			✓	
	D0-06DD1			✓		✓				
	D0-06DD2	✓				✓				
	D0-06DR					✓	✓			
	D0-06DD1-D			✓		✓				
	D0-06DR-D					✓	✓			
	D0-07CDR					✓	✓			
	D0-08CDD1			✓		✓				
	D0-08TR						✓			
	D0-10ND3					✓				
	D0-10TD1				✓					
	D0-10TD2	✓								
	D0-16ND3					✓				
	D0-16TD1				✓					
	D0-16TD2	✓								
	DL105	F1-130AR						✓	✓	
F1-130DR						✓	✓			
F1-130AD				✓				✓		
F1-130DD				✓		✓				
F1-130AA								✓	✓	
F1-130DA						✓			✓	
F1-130DR-D						✓	✓			
F1-130DD-D					✓	✓				
F1-DVNET-AR							✓			
F1-DVNET-DD					✓	✓				
F1-DVNET-DR					✓		✓			



SINKING AND SOURCING CONFIGURATIONS

Sinking/Sourcing Configurations										
	Modules	DC Current Sourcing IN	DC Current Sourcing OUT	DC Current Sinking IN	DC Current Sinking OUT	DC Current Sink/Source IN	AC/DC Current Sink/Source IN	AC/DC Sink/Source (Relay) OUT	AC IN	AC OUT
Ter. Input	T1K-08ND3					✓				
	T1K-16ND3					✓				
	T1K-08NA-1								✓	
	T1K-16NA-1								✓	
Terminator Output	T1K-08TD1				✓					
	T1K-16TD1				✓					
	T1K-08TD2-1		✓							
	T1K-16TD2		✓							
	T1K-16TD2-1		✓							
	T1K-08TA									✓
	T1K-08TAS									✓
	T1K-16TA									✓
	T1K-08TR							✓		
	T1K-16TR							✓		
	T1K-08TRS							✓		
	DL205 Input	D2-08ND3					✓			
D2-16ND3-2						✓				
D2-08NA-1									✓	
D2-08NA-2									✓	
D2-32ND3						✓				
D2-16NA									✓	
D2-08CDR						✓		✓		
D2-32ND3-2						✓				
DL205 Output	D2-04TD1				✓					
	D2-08TD1				✓					
	D2-08TD2		✓							
	D2-32TD2		✓							
	D2-16TD1-2				✓					
	D2-16TD2-2		✓							
	D2-32TD1				✓					
	D2-08TA									✓
	F2-08TA									✓
	D2-12TA									✓
	D2-04TRS							✓		
	D2-08TR							✓		
	F2-08TRS							✓		
	D2-12TR							✓		
	D2-08CDR						✓	✓		



SINKING AND SOURCING CONFIGURATIONS

Sinking/Sourcing Configurations										
	Modules	DC Current Sourcing IN	DC Current Sourcing OUT	DC Current Sinking IN	DC Current Sinking OUT	DC Current Sink/Source IN	AC/DC Current Sink/Source IN	AC/DC Sink/Source (Relay) OUT	AC IN	AC OUT
DL305 Input	D3-08ND2	✓								
	D3-16ND2-1	✓								
	D3-16ND2-2	✓								
	D3-16ND2F	✓								
	F3-16ND3F					✓				
	D3-08NA-1								✓	
	D3-08NA-2								✓	
	D3-16NA								✓	
	D3-08NE3							✓		
D3-16NE3							✓			
DL305 Output	D3-04TD1				✓					
	D3-08TD1				✓					
	D3-08TD2		✓							
	D3-16TD1-1				✓					
	D3-16TD1-2				✓					
	D3-16TD2		✓							
	D3-08TA-1									✓
	D3-08TA-2									✓
	F3-16TA-1									✓
	D3-16TA-2									✓
	D3-08TR							✓		
	F3-08TRS-1							✓		
	F3-08TRS-2							✓		
	F3-08TRS-5							✓		
	D3-16TR							✓		
	D3-04TAS									✓
F3-08TAS									✓	
DL405 Input	F4-08NE3S						✓			
	D4-08ND3S					✓				
	D4-16ND2	✓								
	D4-16ND2F	✓								
	D4-32ND3-1					✓				
	D4-32ND3-2					✓				
	D4-64ND2	✓								
	D4-08NA								✓	
	D4-16NA								✓	
	D4-16NA-1								✓	
	D4-16NE3						✓			
D4-INT	✓		✓		✓					
DL405 Output	D4-08TD1				✓					
	F4-08TD1S				✓					
	D4-16TD1				✓					
	D4-16TD2		✓							
	D4-32TD1				✓					
	D4-32TD1-1				✓					
	D4-32TD2		✓							
	D4-64TD1				✓					
	D4-08TA									✓
	D4-16TA									✓
	D4-08TR							✓		
	F4-08TRS-1							✓		
	F4-08TRS-2							✓		
	D4-16TR							✓		